9.2.1) Given Matthew Jackson PHYS 513 Vn(2) = Vn e-jB= + Vn e jB= HW # 9 November 15,2020 Where Vn(z,t)= Re[Vn(z) eint] similarly Ên(z) = Êt e-jknz + Ê-ejknz En(Z,t) = Re (En(Z) e jut)

Assume  $V_0$  is known. At z=0  $d z=\Delta$ ,  $V \neq T$  are continous. Assume  $V_2=0$  find  $V_0(z)$ ,  $V_1(z)$ , and  $V_2(z)$ . Find  $V_0(z)$  and  $V_1(z)$  and  $V_1(z)$  step 1 break the problem down

$$E_{\circ}^{+} \bigcirc Z_{\circ} \qquad Z_{\circ} \qquad Z_{2}$$

$$\frac{V_{o}^{+}}{Z_{o}} - \frac{V_{o}^{-}}{Z_{o}} = \frac{V_{o}^{-}}{Z_{L}} (1) Z_{L} = Z_{1} + Z_{2} (111)$$

$$V_{o}^{+} + V_{o}^{-} = V_{o}^{-} (11)$$

$$\frac{V_o^+}{Z_o} - \frac{V_o^-}{Z_o} = \frac{V_o^+ + V_o^-}{Z_L}$$

$$\frac{V_o^+ - V_o}{z_o} = \frac{V_o^+ + V_o^-}{z_L}$$

$$V_0 = \frac{(Z_L - Z_0)}{(Z_0 + Z_L)} V_0^+$$

$$V_{0}^{-} = (2_{1}+2_{2}-2_{0}) V_{0}^{+}$$

$$(2_{1}+2_{2}+2_{0})$$

Vise (1) and (11) but (11) rearranged  
to 
$$V_0^- = V_0^L - V_0^+$$

$$\frac{V_o^+}{Z_o} - \frac{V_o^- - V_o^+}{Z_o} = \frac{V_o^-}{Z_L}$$

$$V_{0}^{2} = \frac{2(2,+2z)}{(2-+2,+2z)}$$
  $V_{0}^{+}$ 

$$V_{0}^{5} = V_{1}^{+} = \frac{2(z_{1} + z_{2})}{(z_{0} + z_{1} + z_{2})} V_{0}^{+}$$

$$\frac{V_{1}^{+}}{Z_{1}} - \frac{V_{1}^{-}}{Z_{1}} = \frac{V_{1}^{+} + V_{1}^{-}}{Z_{2}}$$

$$\frac{Z_{1}}{Z_{2}} = \frac{V_{1}^{+} + V_{1}^{-}}{Z_{2}}$$

$$V_{1}^{+} = V_{2}^{+}$$

$$\frac{\left(V_{1}^{+}-V_{1}^{-}\right)}{z_{1}}=\left(\underline{V_{1}^{+}+V_{1}^{-}}\right)$$

$$V_{1}^{-} = \frac{(z_{2}-z_{1})}{(z_{1}+z_{2})}V_{1}^{+}$$

$$V_{1}^{-} = (2_{2} - 2_{1})$$
  $2(2_{1} + 2_{2})$   $V_{0}^{+}$   $(2_{0} + 2_{1} + 2_{2})$ 

$$V_{1} = (2(2_{2}-2_{1}))$$
 $(2_{0}+2_{1}+2_{2})$ 

$$\frac{V_{1}^{+}}{Z_{1}} - \frac{V_{2}^{+} - V_{1}^{+}}{Z_{1}} = \frac{V_{2}^{+}}{Z_{2}}$$

$$\frac{V_{1}^{+}-V_{2}^{+}+(+V_{1}^{+})}{z_{1}}=\frac{V_{2}^{+}}{z_{2}}$$

$$\frac{2V_{1}^{+}-V_{2}^{+}}{z_{1}}=\frac{V_{2}^{+}}{z_{2}}$$

$$Z_{2}(2V_{1}^{+}-V_{2}^{+})=Z_{1}V_{2}^{+}$$
  
 $2V_{1}^{+}Z_{2}=V_{2}^{+}(Z_{1}+Z_{2})$   
 $V_{2}^{+}=\frac{2Z_{2}}{(Z_{1}+Z_{2})}$ 

$$V_{z}^{+} = \frac{2z_{z}}{(z_{1}+z_{2})} \frac{2(z_{1}+z_{2})}{(z_{0}+z_{1}+z_{2})} V_{0}^{+}$$

$$V_{2}^{+} = 4 z_{2}$$
 $(z_{1}+z_{2}+z_{3})$ 

$$\frac{\sqrt{5}}{\sqrt{5}} = \frac{(2.+2z-2.)}{(2.+2z+2.)}$$

$$\frac{V_1^-}{V_1^+} = \frac{(Z_2 - Z_1)}{(Z_1 + Z_2)}$$

9.2.2.1) Show Mathew Jackson PHYS 513 HW # 9 V(2,t)= V+[cos (Wt-Bz) November 16,2020 + p cos (wt + Bz) | Can be written tuo standing waves V(Zit) = Acos (wt) cos (Bz) + Bsin (wt) sin (BZ) and Find A + B cos (wt -Bz) - cos (u-V) cos (wt + Bz) > cos (M+V) COS (M-V)= COS M COS V + SINMSIN V (1) cos (utV) = cos u cos V- sin usin V (11) (1) + (11) = 2 cosucos V = cos(u-V) + cos(u+V)

(1)-(11) = 2 sin MS(n V = cos(u-V)-cos(m+V)

define 
$$V = V + (V - P) = 1$$
 $V(z,t) = V + (V + (V - P)) \cos(u - V) + (V + (P - V)) \cos(u + V)$ 
 $= V + (V + (P - V)) \cos(u + V) + (V + (V - V)) +$ 

9.2.23) The plot generated from the Code creates a standing wave with Vmax and Vmin. These Vmax and Vmin relate to the two standing waves found in part 9.2.1 by the relationship of the ( oefficients (1-p) and (1+p). 24 p<0 |(1-p)) - (1+1p1) and [(1+p)] → (1-1p1). There Fore, the standing ware rate is given by  $S = \frac{1+|\rho|}{1-|\rho|}$ 

IPI can be determined from the plot of the rections, and if the reflected wave is given, so can the sign.