11.2.1) Using Plots Matthew Jackson Final Part 2 (HWII) PH45 513 labeled Final_Part_II_1_ December 2020 From the plots with the above name, one Can see that the approximation holds fairly with the inputs 10=1V, L=1H; C=1F, W=0,0055-1 and N=1000. The 2 of the transmission line is given by the relation B= Ztt = WVLC (page 230 (7)) which yeilds a wave length of ~ 1257 m (or nodes). with this extremely long warme length, the differences in the solution very by a maximum 0.52% for Voltage, 0.46% for current, and 0.25% for impedance. It should be noted that the impedance of the analytical solution is Z= 14c as opposed to' 7= 1/c-WL)2 as discussed in the paper

The Analytical solution displayed comes from
the equations shown in HW #9, specifically

V(v)- ii+(-jBnx [1, ~, 17)

$$\tilde{V}_{n}(x) = \tilde{V}_{n}^{+}(e^{-jB_{n}x}\left[1+\tilde{\rho}(x)\right])$$

$$\widetilde{\zeta}_n(x) = \frac{\widetilde{V}_n(x)}{\widetilde{T}_n(x)}$$

and
$$p(x) = \frac{z_2 - z_1}{z_1 + z_1} e^{-2jB_n x}$$

Given how similar the answers are, I, assert that this is a good approximation. When $E_L = Z_- O$

(These plots can be generated with ANIMATE variable and the Z-L whale)

11.2.2) Using Plots labelled Final_Part_ II - 2-* From the above plots, much like the other Section, the Analytical and Ladder circuit align nicely, When the Iload Empedance is set to 3 14c, the solutions have a mismatch of 0,0069 in voltage, 0.015 in current, and 0.0017 In impedance. The Error is rather comparable When looking at a load impedance of 10 M/c. (final - Part - II - 2 - 2. pdf). Lastly, When supplying a more interesting impudance of 2+2j as the load, the accuracy of volves is 0.04 for voltage, 0.043 for current, and 0.005 for impedance.

Since the impedance, current, and voltage align so well. I tell conholient stating the Ladder circuit works well as an approximation it a transmission line.