

11.1.1) Show the following

Matthew Jackson  
PHYS 513  
Final (HW #11)  
December 2020

$$\tilde{V}_1 = \tilde{V}_0 - j\omega L \tilde{I}_1$$

$$\tilde{I}_2 = \tilde{I}_1 - j\omega C \tilde{V}_1$$

$$\tilde{V}_2 = \tilde{V}_1 - j\omega L \tilde{I}_2$$


$$\tilde{I}_2 = \frac{\tilde{V}_2}{Z_L}$$

Remember source is

$$V_0 \cos(\omega t) = \text{Re}[\tilde{V}_0]$$

Circuit on page 2

Start with first inductor in loop 1

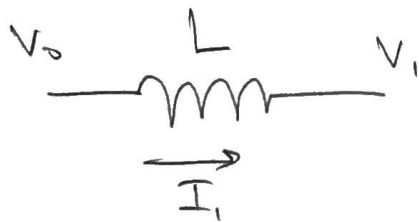

$$\Delta \tilde{V}_0 = L \frac{d\tilde{I}_1}{dt}$$


$$\tilde{V}_0 - \tilde{V}_1 = L \frac{d\tilde{I}_1}{dt}$$

$$\tilde{V}_0 - \tilde{V}_1 = L(j\omega \tilde{I}_1)$$

$$\tilde{V}_1 = \tilde{V}_0 - j\omega L \tilde{I}_1$$

$$\frac{d\tilde{I}_1}{dt} = \frac{d}{dt} (\overset{\text{const}}{\tilde{I}_1'} e^{j\omega t})$$
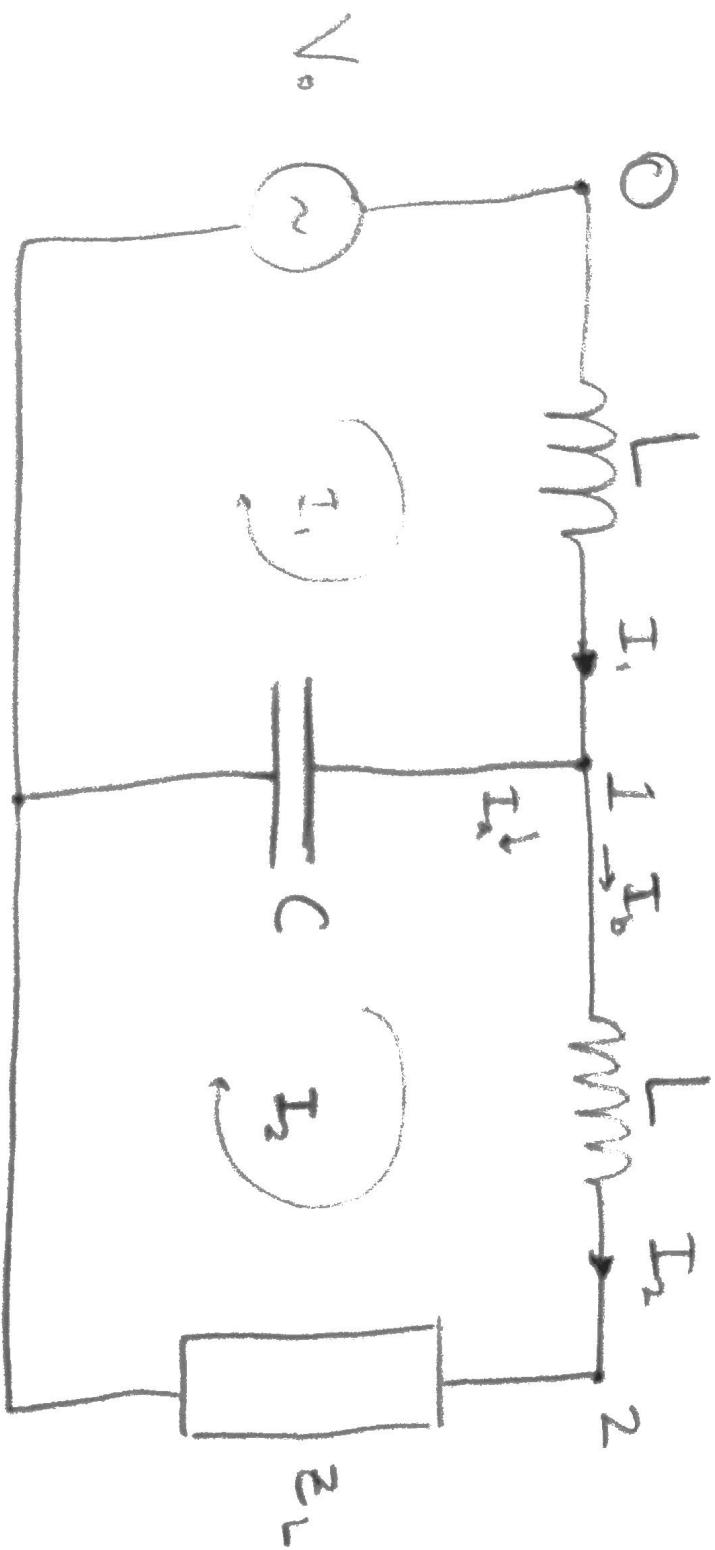
$$\frac{d\tilde{I}_1}{dt} = \tilde{I}_1' e^{j\omega t} j\omega$$



Inductor in second loop (loop 2)

$$\Delta \tilde{V}_{12} = L \frac{d\tilde{I}_2}{dt}$$

$$\frac{d\tilde{I}_2}{dt} = \frac{d}{dt} \left( \tilde{I}_2' e^{j\omega t} \right)$$


$$\tilde{V}_1 - \tilde{V}_2 = L \frac{d\tilde{I}_2}{dt}$$

$$\frac{d\tilde{I}_2}{dt} = \tilde{I}_2' e^{j\omega t} j\omega$$

$$\tilde{V}_1 - \tilde{V}_2 = L(j\omega \tilde{I}_2)$$

$$\tilde{V}_2 = \tilde{V}_1 - j\omega L \tilde{I}_2$$


Look at Node 1

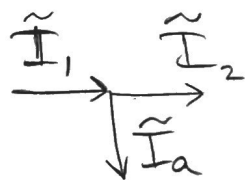

$$\tilde{I}_1 - \tilde{I}_2 - \tilde{I}_a = 0$$

$$\tilde{I}_1 - C(j\omega \tilde{V}_1) = \tilde{I}_2$$
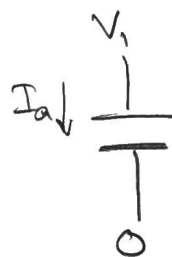
$$\tilde{I}_2 = \tilde{I}_1 - j\omega C \tilde{V}_1$$



$$\tilde{I}_a = C \frac{d\tilde{V}_1}{dt}$$

$$I_a = C \frac{d}{dt} \left( \tilde{V}_1' e^{j\omega t} \right)$$

$$I_a = C(j\omega \tilde{V}_1' e^{j\omega t})$$



11.1.2)  $\tilde{V}_0 = V_0$  and previous equations,

Solve for  $Z_1$  and  $Z_0$  where  $Z_1$  &  $Z_0$  are

$Z_1$

and

$Z_0$

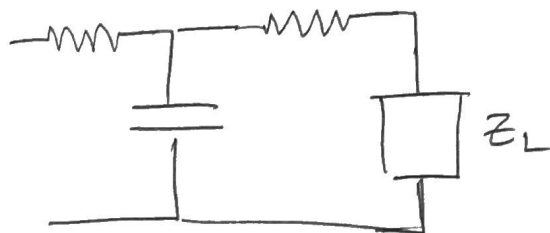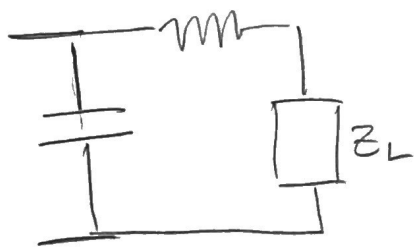

$Z_1 \rightarrow$  Capacitor  $\parallel$  (Inductor &  $Z_L$ )

$\rightarrow$  Capacitor  $\parallel Z_a$

$$Z_a = j\omega L + Z_L$$

$$(Z_1)^{-1} = \left( \frac{-j}{\omega C} \right)^{-1} + (j\omega L + Z_L)^{-1}$$

$$(Z_1)^{-1} = j\omega C + \frac{1}{j\omega L + Z_L}$$

$$(Z_1)^{-1} = \frac{j\omega C(j\omega L + Z_L) + 1}{(j\omega L + Z_L)}$$

$$Z_1 = \frac{(j\omega L + Z_L)}{j\omega C(j\omega L + Z_L) + 1}$$

$$Z_1 = \frac{(j\omega L + Z_L)}{-\omega^2 CL + j\omega C Z_L + 1}$$

← this is also useful

$$Z_1 = \frac{(j\omega L + Z_L)}{(1 - \omega^2 CL) + j\omega C Z_L} * \frac{(1 - \omega^2 CL) - j\omega C Z_L}{(1 - \omega^2 CL) - j\omega C Z_L}$$

wolfram alpha

$$Z_1 = \frac{-j(CL^2\omega^3 + C\omega Z_L^2 + L\omega)}{(1 - \omega^2 CL)^2 + \omega^2 C^2 Z_L^2}$$

$$Z_0 = j\omega L + Z_1$$

$$= j\omega L +$$

wolfram alpha again

$$Z_0 = \frac{j(C^2 L^3 \omega^5 + C^2 L \omega^3 Z_L^2 - 3CL^2 \omega^3 - C\omega Z_L^2 + 2L\omega)}{(1 - \omega^2 CL)^2 + \omega^2 C^2 Z_L^2} + Z$$

Alternative form straight from  
wolfram alpha (this makes section  
3 easier)

This is what got plugged into  
wolfram alpha

$$Z_0 = jL\omega + \frac{1}{j\omega + \frac{1}{Z_L + jL\omega}}$$

← series  
parallel
← series

wolfram solution

$$Z_0 = \frac{-jCL^2\omega^3 - CL\omega^2 Z + jZL\omega + Z_L}{-CL\omega^2 + jC\omega Z_L + 1}$$

↗  
this is the same  
as the other solution

11.1.3) Using the previous solve for

1.)  $\tilde{I}_k$  for  $k=1,2$  and  $\tilde{V}_k$  for  $k=1,2$

Put everything in terms of  $\tilde{V}_0 + Z_0$

$$\underline{\tilde{I}_1 = \frac{\tilde{V}_0}{Z_0}}$$

$$\tilde{V}_1 = \tilde{V}_0 - j\omega L \tilde{I}_1$$

$$\underline{\tilde{V}_1 = \tilde{V}_0 - j\omega L \frac{\tilde{V}_0}{Z_0}}$$

$$\tilde{I}_2 = \tilde{I}_1 - j\omega C \tilde{V}_1$$

$$\underline{\tilde{I}_2 = \frac{\tilde{V}_0}{Z_0} - j\omega C \left( \tilde{V}_0 - j\omega L \frac{\tilde{V}_0}{Z_0} \right)}$$

$$\tilde{V}_2 = \tilde{V}_1 - j\omega L \tilde{I}_2$$

$$\underline{\tilde{V}_2 = \tilde{V}_0 - j\omega L \frac{\tilde{V}_0}{Z_0} - j\omega L \left( \frac{\tilde{V}_0}{Z_0} - j\omega C \left( \tilde{V}_0 - j\omega L \frac{\tilde{V}_0}{Z_0} \right) \right)}$$

$$\tilde{I}_1 = \tilde{V}_0 \left( \frac{1}{Z_0} \right)$$

$$\tilde{V}_2 = \tilde{V}_0 \left( 1 - \frac{j\omega L}{Z_0} - j\omega L \left( \frac{1}{Z_0} - j\omega C \left( 1 - \frac{j\omega L}{Z_0} \right) \right) \right)$$

$$\tilde{V}_1 = \tilde{V}_0 \left( 1 - \frac{j\omega L}{Z_0} \right)$$

$$\tilde{I}_2 = \tilde{V}_0 \left( \frac{1}{Z_0} - j\omega C \left( 1 - \frac{j\omega L}{Z_0} \right) \right)$$

$$\tilde{I}_1 = V_0 \left( \frac{1}{z_0} \right)$$

$$= V_0$$



Verify Answer by solving for  $Z_0$

using  $\tilde{I}_2 = \tilde{V}_0 \left( \frac{1}{Z_0} - j\omega c \left( 1 - \frac{j\omega L}{Z_0} \right) \right)$  and

$$\tilde{I}_2 = \frac{\tilde{V}_2}{Z_L} = \frac{\tilde{V}_0}{Z_L} \left( 1 - \frac{j\omega L}{Z_0} - j\omega L \left( \frac{1}{Z_0} - j\omega c \left( 1 - \frac{j\omega L}{Z_0} \right) \right) \right)$$

and solving for  $Z_0$  (should be the same as original  $Z_0$  in section 2)

$$\cancel{\tilde{V}_0} \left( \frac{1}{Z_0} - j\omega c \left( 1 - \frac{j\omega L}{Z_0} \right) \right) =$$

$$\cancel{\tilde{V}_0} \frac{1}{Z_L} \left( 1 - \frac{j\omega L}{Z_0} - j\omega L \left( \frac{1}{Z_0} - j\omega c \left( 1 - \frac{j\omega L}{Z_0} \right) \right) \right)$$

$$Z_L \left( \frac{1}{Z_0} - \left( j\omega c + \frac{\omega^2 c L}{Z_0} \right) \right) =$$

$$1 - \frac{j\omega L}{Z_0} - j\omega L \left( \frac{1}{Z_0} - \cancel{j\omega c} + \frac{\omega^2 c L}{Z_0} \right)$$

$$Z_L \left( \frac{1}{Z_0} - j\omega c - \frac{\omega^2 c L}{Z_0} \right) =$$

$$1 - \frac{j\omega L}{Z_0} - \left( \frac{j\omega L}{Z_0} + \omega^2 c L - \frac{j\omega^3 c L^2}{Z_0} \right)$$

$$Z_L \left( \frac{1}{Z_0} - j\omega C - \frac{\omega^2 CL}{Z_0} \right) =$$

$$1 - \frac{j\omega L}{Z_0} - \frac{j\omega L}{Z_0} - \omega^2 CL + \frac{j\omega^3 CL^2}{Z_0}$$

$$\frac{Z_L}{Z_0} - \frac{\omega^2 CL Z_L}{Z_0} + \frac{2j\omega L}{Z_0} - \frac{j\omega^3 CL^2}{Z_0} =$$

$$j\omega C Z_L + 1 - \omega^2 CL$$

$$\frac{Z_L - \omega^2 CL Z_L + 2j\omega L - j\omega^3 CL^2}{Z_0} =$$

$$j\omega C Z_L + 1 - \omega^2 CL$$

$$Z_0 = \frac{Z_L - \omega^2 CL Z_L + 2j\omega L - j\omega^3 CL^2}{j\omega C Z_L + 1 - \omega^2 CL} \quad \checkmark$$


same  $Z_0$  from both methods

(this solution matches the wolfram solution)


11.1.4) Using the N ladder circuit, solve the following

1.) Write an iterative equation for  $Z_{n-1}$  in terms of  $Z_n$ ,  $\omega$ ,  $L$ , and  $C$

Look at a single node then generalize

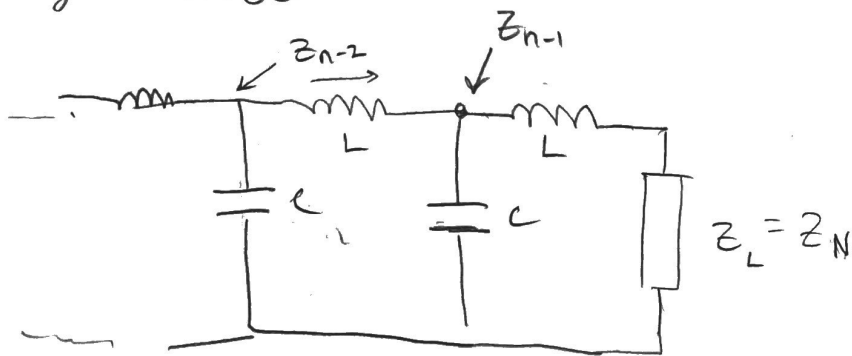

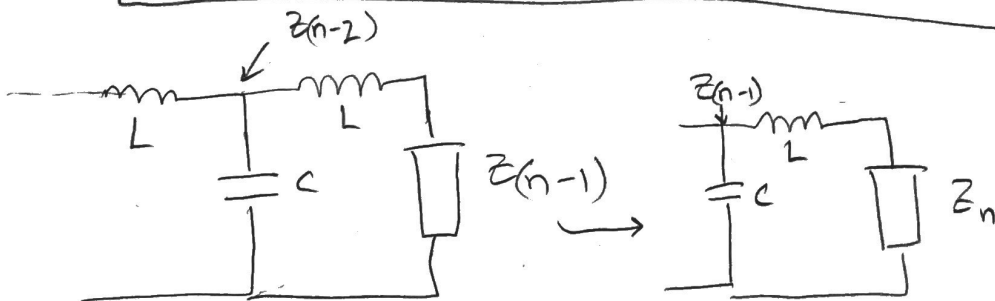
$$Z_{n-1} = \left( j\omega C + (Z_n + j\omega L)^{-1} \right)^{-1}$$



2.) Write an equation that relates  $\tilde{V}_{n+1}$  to  $\tilde{V}_n$  and  $\tilde{I}_n$

Use the same as last section

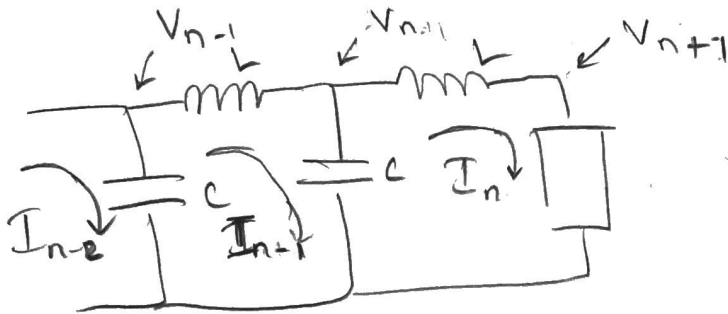


$$V_n - V_{n+1} = L \frac{dI_n}{dt}$$

$$\frac{dI}{dt} = j\omega I$$

$$V_{n-1} - V_n = L \frac{dI_{n-1}}{dt}$$

$$\tilde{V}_{n+1} = \tilde{V}_n - j\omega L \tilde{I}_n$$

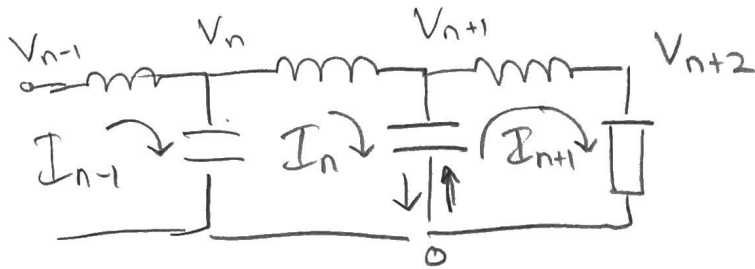3.) Write an equation that relates  $\tilde{I}_{n+1}$  to  $\tilde{I}_n$  and  $\tilde{V}_{n+1}$




$$\tilde{I}_n - \tilde{I}_{n+1} = C \frac{d\tilde{V}_{n+1}}{dt}$$

$$\frac{d\tilde{V}}{dt} = j\omega \tilde{V}$$

$$\tilde{I}_{n+1} = \tilde{I}_n - j\omega C \tilde{V}_{n+1}$$

Voltage across  $Z_L$

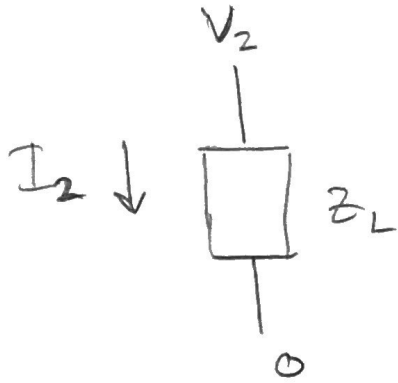

$$V_2 = I_2 Z_L$$

$$I_2 = \frac{V_2}{Z_L}$$